

## CMPE 101 Laboratory Exercise 2

### Ohm's Law

Nicholas Curl

Partner: Kevin Kuzmeski

Performed: 9/5/18

Submitted: 9/19/18

Lab Section: 4

Instructor: Joseph Gallina

TA: Michael, Tommy, Ezra

Lecture Section: 1

Professor: Schanchieh Yang and Gordon  
Werner

By submitting this report, you attest that you neither have given nor have received any assistance (including writing, collecting data, plotting figures, tables or graphs, or using previous student reports as a reference), and you further acknowledge that giving or receiving such assistance will result in a failing grade for this course.

Your Signature: \_\_\_\_\_

# Abstract

The purpose for this exercise was to use Ohm's law to demonstrate how current run though a circuit. The problem was to calculate the amount of resistance within a circuit with three different resistors being used. Each resistor had a different level of resistance. A multimeter was used to measure the amount of current and voltage was running through each resistor and the whole circuit.

## Design Methodology

Three resistors of different resistances were used during the exercise. Each resistance was determined from the banded reading, then were measured using a multimeter to determine the true resistance. The resistances of each resistor of its rated resistance, rated tolerance, and the actual resistance are shown in Table 1.

Table 1: *Rated Resistance, Rated Tolerance, and Actual Resistance*

	Rated Resistance ( $\Omega$ )	Rated Tolerance (%)	Actual Resistance ( $\Omega$ )
R <sub>1</sub>	3,300	5	3,233
R <sub>2</sub>	15,000	5	14,590
R <sub>3</sub>	27,000	5	26,982

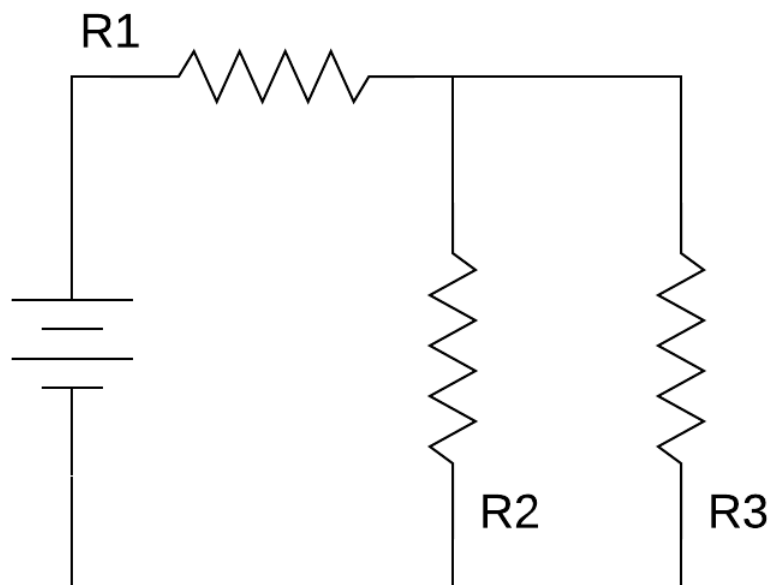


Figure 1: Schematic of the circuit setup

A circuit was constructed using based off the schematic shown in Figure 1. With the circuit built, the voltages were measured across Power Supply, Resistor 1 and Resistor 2. Voltage measurements were taken across each component from a range of 2V-5V and recorded (See Table 2).

Table 2: *Voltages of the Power Supply, Resistor 1 and Resistor 2*

$V_{PS}$ (V)	$V_{R1}$ (V)	$V_{R2}$ (V)
2	0.5	1.5
2.99	0.75	2.25
3.99	1	2.99
4.99	1.26	3.74

After the voltages were measured, the multimeter was reconfigured to measure the current through all three resistors and was recorded (See Table 3).

Table 3: *Currents through Resistor 1, Resistor 2, and Resistor 3*

$I_{R1}$ (mA)	$I_{R2}$ (mA)	$I_{R3}$ (mA)
0.39	0.25	0.14

The equivalent resistor was calculated for the two parallel resistors using eq. 1, then an equivalent circuit was then drawn (See Figure 2).

$$\frac{1}{R_{EQ}} = \frac{1}{R_2} + \frac{1}{R_3} \quad (1)$$

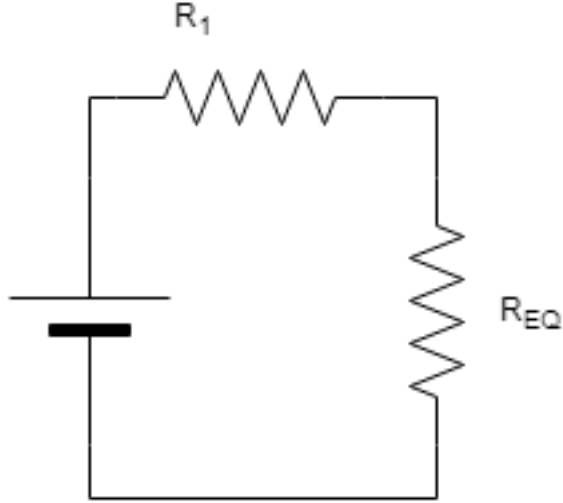


Figure 2: Equivalent circuit schematic for parallel resistors

The equivalent resistor for the two parallel resistors were calculated to be  $9,642.86 \, \Omega$ . The total equivalent resistor for the entire circuit was calculated using eq. 2, then a equivalent circuit was drawn for the new equivalent resistor (See Figure 3).

$$R_{EQ} = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} \quad (2)$$

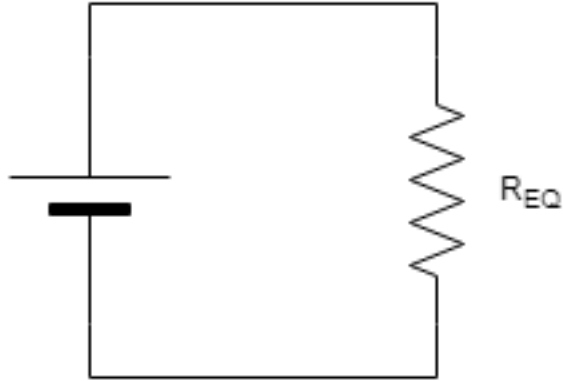


Figure 3: Equivalent circuit schematic for entire circuit

The new equivalent resistor was calculated to be  $12,942.9 \, \Omega$ . Voltages were calculated based on the measured currents at 5V for the power supply, Resistor 1, Resistor 2 using eq. 3.

$$V = IR \quad (3)$$

The calculated voltages are as follows:  $V_{PS}=5.05$  V,  $V_{R1}=1.287$  V, and  $V_{R2}=3.75$  V.

## Results and Analysis

The data recorded was placed into a table (See Table 4) and using the data, a graph of the voltage vs current was created for Resistor 3 as shown in Figure 4.

Table 4: *Voltages of the power supply and the three resistors and the current for each resistor*

$V_{PS}$ (V)	$V_{R1}$ (V)	$V_{R2}$ (V)	$V_{R3}$ (V)	$I_{R1}$ (mA)	$I_{R2}$ (mA)	$I_{R3}$ (mA)
2	0.5	1.5	1.5	0.16	0.46	0.06
2.99	0.75	2.25	2.25	0.23	0.15	0.08
3.99	1	2.99	2.99	0.30	0.20	0.11
4.99	1.26	3.74	3.74	0.39	0.25	0.14

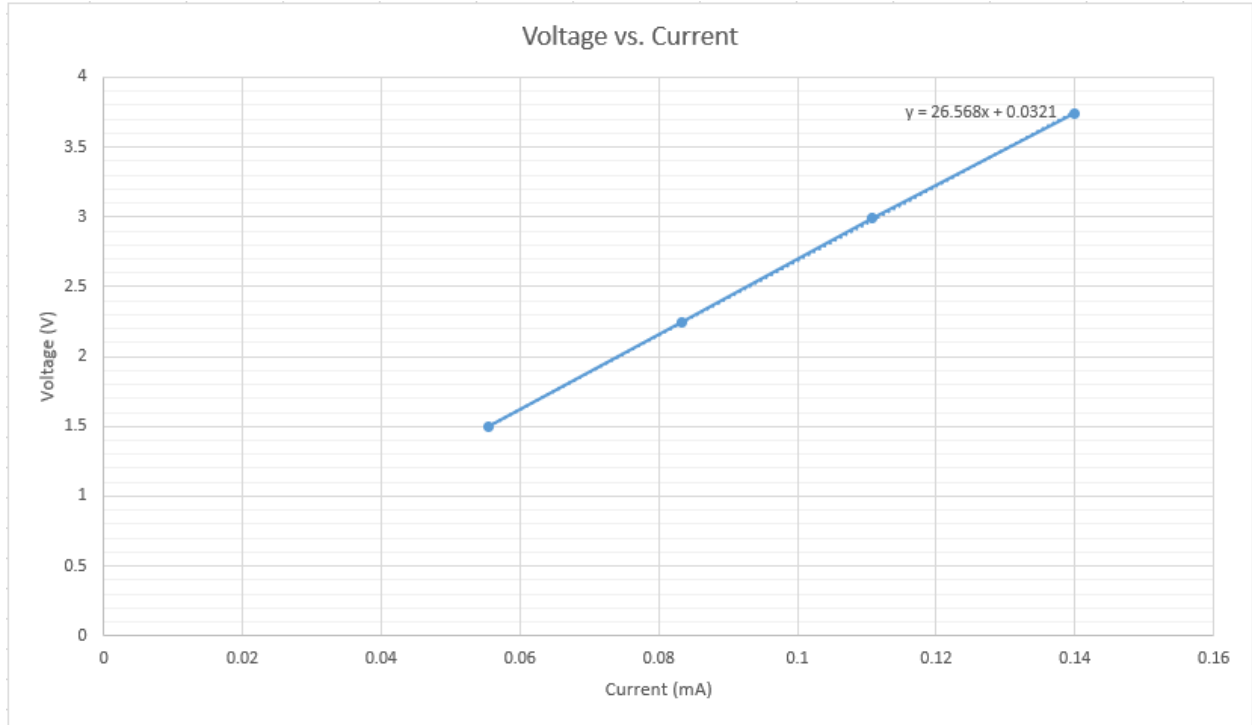


Figure 4: Graph of Voltage VS Current of Resistor 3

The slope of the graph represents the resistance of Resistor 3 using eq. 4 as the equation.

$$\frac{V_{R3}}{I_{R3}} = \Omega_{R3} \quad (4)$$

The slope of the line for Resistor 3 was able to approximate the true value of the resistor with a percent error of 1.53%.

## Conclusion

Ohm's Law proves that the amount of voltage is proportional to the amount of current running through the circuit. Using a breadboard with a simple parallel circuit with the multimeter. It allows for easy measurement of each value of the resistors, the voltage, and the current of the circuit. As a result, Figure 2 shows that the more voltage put into the circuit the stronger the current becomes. When the voltage was lower the current was proportionally lower. When one was raised the other raised with it. The exercise proved successful in showing how current and voltage are proportional due to Ohm's Law